

Amplifier characterization

Ideal Behavior and Manifestation of Errors



Anton J.M. Montagne

Perscitech

September 29, 2018

Introduction

Amplifier: the concept

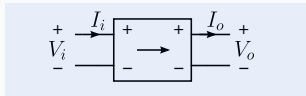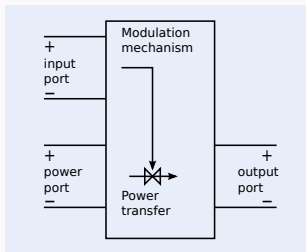

- Amplifiers provide their load (observer) with an accurate copy of their source signal, while they increase the *available power* to the load
- The load power is primarily obtained from a power source
- The amplification mechanism is embodied in *active devices*
- Ideal functional behavior: conceptual amplifier is modeled as a two-port:
 - Linear
 - Instantaneous
 - Time-invariant (if fixed transfer)
 - Time-variant (if time-dependent transfer)

Physical behavior: error sources

- Real-world amplifier = multi-port:
 - Undesired transfer to and from power port
- Violation of port constraints:
 - Non-ideal port isolation
- Noise limitation:
 - Deterioration of signal-to-noise ratio
- Power and speed limitation:
 - Nonlinear, dynamic behavior causes signal distortion.

Introduction

Amplifiers: Manifestation of errors and Performance specification

Introduction

Amplifier types

Modeling of non-ideal behavior

Manifestation of errors depends on

- Applied technology
- Way in which the information is embedded in the signal
- Observer's sensitivity to specific information processing errors

Performance specification

- Desired functional (two-port) behavior
- Undesired transfer from and to power port
- Manifestation errors due to fundamental physical limitations, interference sources and environmental changes, ageing, ...
- Specification of power source(s).

Introduction

Amplifiers: Environmental specification and cost factors

Environment

- Temperature
- Humidity
- Shock and vibrations
- EMI sources
- Any physical property of the environment that may affect the signal processing quality
- May relate to any life cycle process (not only operation)

Cost factors

- Space
- Weight
- Available power
- May relate to any life cycle process (not only operation)

Amplifier types

Selection of port quantities

Selection of port quantities

- In case of sensors and actuators:
 - The electrical quantity (current or voltage) that shows the best reproducing relation to the transducer's input/output physical quantity.
- In case of interconnected electronic circuits:
 - Distribution with common-ground: voltage
 - Combination with common ground: current
 - Dominant parasitic impedances in parallel with the signal path: current
 - Dominant parasitic impedances in series with the signal path: voltage.

Amplifier types

Overview port impedance requirements

Nine unilateral amplifier types:


- ① Amplifier's input impedance independent of load impedance
- ② Amplifier's output impedance independent of source impedance

no	source quantity	load quantity	Z_i	Z_o
1	voltage	voltage	∞	0
2	voltage	current	∞	∞
3	voltage	voltage or current	∞	Z_{charo}
4	current	voltage	0	0
5	current	current	0	∞
6	current	voltage or current	0	Z_{charo}
7	voltage or current	voltage	Z_{chari}	0
8	voltage or current	current	Z_{chari}	∞
9	voltage or current	voltage or current	Z_{chari}	Z_{charo}

Amplifier types


Characterization of ideal functional behavior

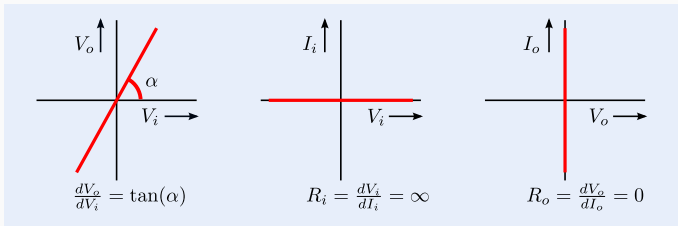- Port v-i characteristics
 - Modeled by v-i characteristics of input and output port
 - Linear, time-invariant, instantaneous
- Transfer characteristics:
 - Desired transfer from input port to output port
 - Linear, time-invariant, instantaneous
- Example voltage amplifier:



Amplifier types

Port isolation

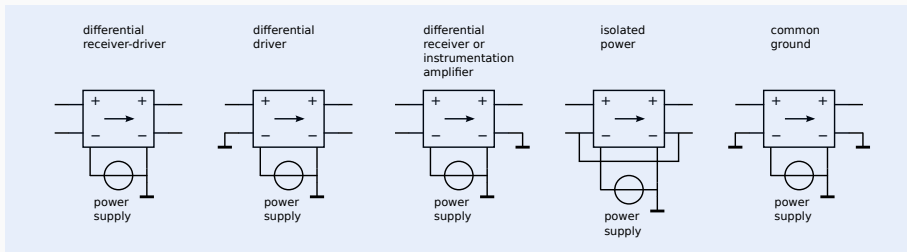

Port isolation configurations


- ① Floating source and load
- ② Grounded source, floating load
- ③ Grounded load, floating source
- ④ Floating source and load with common
- ⑤ Grounded source and load

Amplifier types

Modeling of functional behavior

Two-port representation with transmission-1 matrix
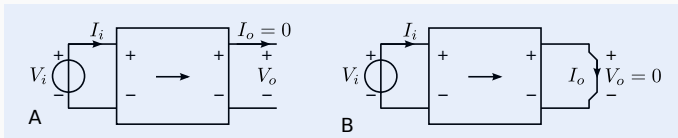
$$\begin{pmatrix} V_i \\ I_i \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_o \\ I_o \end{pmatrix}$$



$$A = \frac{1}{\mu} = \left. \frac{V_i}{V_o} \right|_{I_o=0}$$

$$C = \frac{1}{\zeta} = \left. \frac{I_i}{V_o} \right|_{I_o=0}$$


$$B = \frac{1}{\gamma} = \left. \frac{V_i}{I_o} \right|_{V_o=0}$$

$$D = \frac{1}{\alpha} = \left. \frac{I_i}{I_o} \right|_{V_o=0}$$

Amplifier types

Source-load transfer

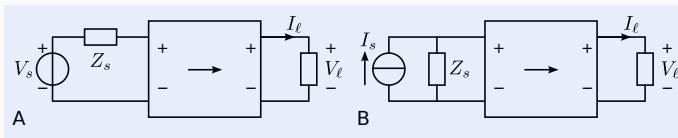Source-load transfer expressed in transmission parameters:



Source-load transfers expressed with matrix parameters and Z_s and Z_l :


$$A_v = \frac{V_l}{V_s} = \frac{1}{A + B\frac{1}{Z_l} + CZ_s + D\frac{Z_s}{Z_l}}, \quad A_y = \frac{I_l}{V_s} = \frac{1}{AZ_l + B + CZ_l Z_s + DZ_s}$$

$$A_z = \frac{V_l}{I_s} = \frac{1}{A\frac{1}{Z_s} + B\frac{1}{Z_s Z_l} + C + D\frac{1}{Z_l}}, \quad A_i = \frac{I_l}{I_s} = \frac{1}{A\frac{Z_l}{Z_s} + B\frac{1}{Z_s} + CZ_l + D}$$

Amplifier types

Driving-point impedances

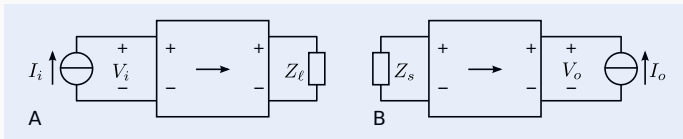Port impedances expressed in transmission parameters:




Port impedances expressed with matrix parameters and Z_s and Z_ℓ :

$$Z_i = \frac{V_i}{I_i} = \frac{AZ_\ell + B}{CZ_\ell + D} \quad Z_o = \frac{V_o}{I_o} = \frac{DZ_s + B}{CZ_s + A}$$

Amplifier types

Available power gain

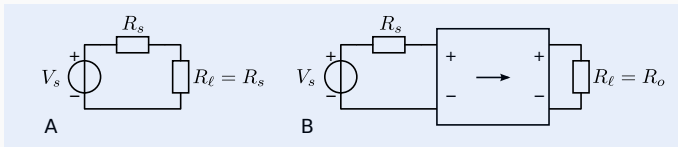Available power gain expressed in transmission parameters:



Source available power:

$$P_{S,Av} = \frac{V_s^2}{4 \operatorname{Re}(Z_s)}$$

Output port available power:

$$P_{O,Av} = \frac{V_o^2}{4 \operatorname{Re}(Z_o)}$$

Available power gain two-port; instantaneous case:

$$G_p = \frac{P_{O,Av}}{P_{S,Av}} = \frac{1}{AD + AB/R_s + BC + CDR_s}$$

Amplifier types

Conclusions modeling functional behavior

Transmission parameters of unilateral amplifier types:

no	Z_i	Z_o	A	B	C	D
1	∞	0	A	0	0	0
2	∞	∞	0	B	0	0
3	∞	Z_{char}	A	B	0	0
4	0	0	0	0	C	0
5	0	∞	0	0	0	D
6	0	Z_{char}	0	0	C	D
7	Z_{char}	0	A	0	C	0
8	Z_{char}	∞	0	B	0	D
9	Z_{chari}	Z_{charo}	A	B	C	D

Unilateral: $AD = BC$

Error modeling

Modeling of non-ideal port isolation and power supply transfer

Non-ideal port isolation

- A real-world amplifier does not behave as a natural two-port:
 - physical amplifier = multi-port:
 - transmission from and to power supply
 - violation of port constraints:
 - non-ideal port isolation


Modeling requires description of amplifier as multi-terminal network.

- Often incomplete specification of the amplifier's behavior

Error modeling

Modeling of non-ideal port isolation

Non-ideal port isolation (input-output)

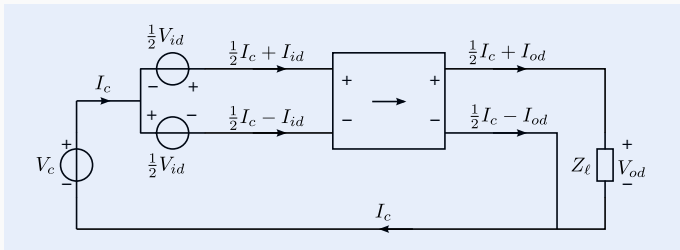

- Requires five extra parameters
- Usually only two parameters are modelled:


$$CMRR_V = \frac{V_{id}}{V_{cm}}, \quad Z_{cm} = \frac{V_{cm}}{I_{cm}}$$

- Only complete with specified source and load impedances.

Error modeling

Modeling of non-ideal power-supply

Non-ideal power-supply isolation

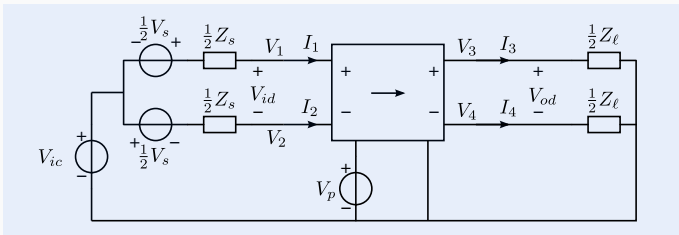

- Requires 19 extra parameters
- Usually only two extra parameters are modelled:

$$PSRR = \frac{V_{id}}{V_{cc}}, \quad F = \frac{V_{od}}{V_{id}} \frac{V_{ic}}{V_{oc}}$$