

Principle of Amplification

Application of Nonlinear Devices and Power Sources

Anton J.M. Montagne

Perscitech B.V.

September 25, 2017

Introduction

Aim of this lecture

Introduction

Nonlinear
two-terminal
resistors

Nonlinear
multi-terminal
resistors



- ① Understand the amplification mechanism embodied in 'active devices'
 - Vacuum tubes, BJTs, FETs and MOSFETs are passive devices
 - Combinations of the above devices and power sources may result in *active* behavior
 - Active network element delivers power to passive network element
 - Passive element: product of branch voltage and branch current is positive
 - Active element: product of branch voltage and branch current is negative
- ② Understand the concept of biasing
 - Available power gain of biased stage may exceed unity: load signal power mainly provided by bias sources
 - Device properties and quiescent operating point determine amplifying capabilities
 - Conceptual biasing with ideal voltage and current sources only
 - Design of biasing circuitry separated from design of signal processing

Two-terminal resistive elements

V-I Characteristics

Voltage and current-controlled notation

Symbol

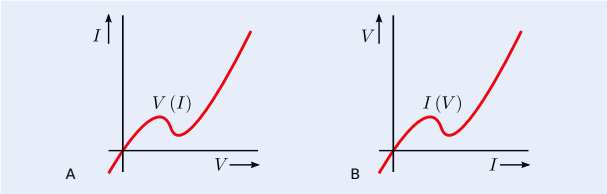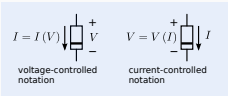


Voltage-controlled and current-controlled representation of the $v - i$ characteristics of a passive two-terminal resistive element.

Two-terminal resistive elements

Examples

element	parameters	current-controlled	voltage controlled
linear resistor	R	$V(I) = IR$	$I(V) = \frac{V}{R}$
voltage source	V	$V(I) = V$	$I(V) : \text{undefined}$
current source	I	$V(I) : \text{undefined}$	$I(V) = I$
ideal diode	I_S, U_T	$V(I) : V_T \ln \left(1 + \frac{I}{I_S} \right)$ valid for $I > -I_S$	$I(V) : I_S \exp \left(\frac{V}{U_T} \right)$

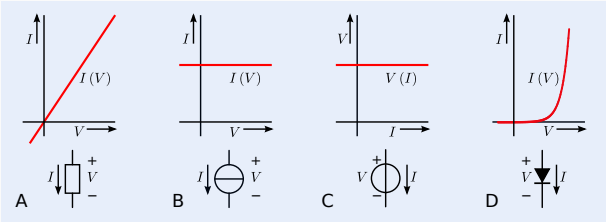

Two-terminal resistive elements

Complementary devices


$v - i$ **Characteristics of complementary devices:**

$$R_1 : V = V(I) \quad \text{or} \quad I = I(V)$$

$$R_2 : V = V_c(I) \quad \text{or} \quad I = I_c(V)$$

R_1 and R_2 are said to be complementary if:
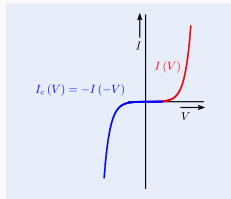
$$V_c(i) = -V(-I) \quad \text{or} \quad I_c(V) = -I(-V)$$



Two-terminal resistive elements

Operating point and biasing

Selection of operating point (V_Q, I_Q)

v = voltage deviation from V_Q

i = current deviation from I_Q


$$I_Q + i = I(V_Q + v); \text{ voltage-controlled representation}$$

$$V_Q + v = V(I_Q + i); \text{ current-controlled representation}$$

Two-terminal resistive elements

Operating point and biasing

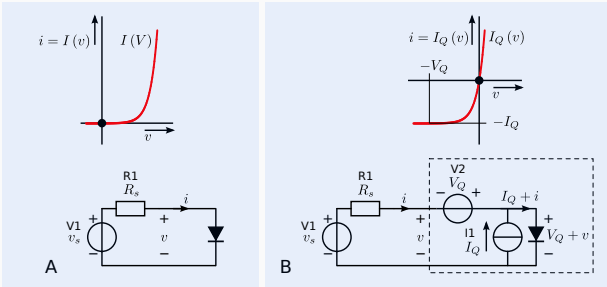Fix operating point with a bias voltage and a bias current source:



Two-terminal resistive elements

Dependent and independent bias sources and biasing errors

Dependent and independent bias sources

- Either the bias voltage or the bias current can be selected by design
- The other follows from the selected one and the devices $V - I$ characteristic at the operating temperature

Biasing errors

- $V - I$ characteristic of the device is not fully known
- $V - I$ characteristic of the device is subjective to temperature changes
- Implementation of biasing sources not without errors

If biasing errors become too large, error-reduction techniques have to be applied. This will be discussed at a later stage.

Two-terminal resistive elements

Linearization in the operating point

The $v - i$ relation of the biased non-linear device can be written as:

$$I = I_Q(V) \text{ with: } I_Q(V) = I(V_Q + v)$$
$$V = V_Q(I) \text{ with: } V_Q(\tilde{i}) = V(I_Q + i)$$


Small-signal behavior:

- For small deviations from the operating point, the characteristics can be considered linear.
- The small-signal characteristics in the operating point Q are:

$$i = g.v; \quad g = \left. \frac{I_Q(v)}{dv} \right|_{v=0}$$
$$v = r.i; \quad r = \left. \frac{V_Q(i)}{di} \right|_{i=0}$$

Two-terminal resistive elements

Available power gain

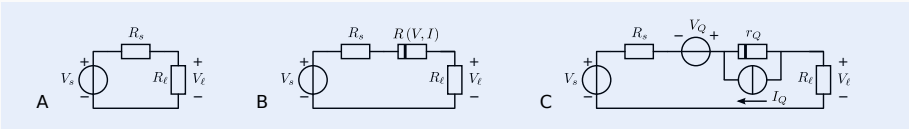

- Available power gain = ratio of available power at the output port of the amplifier and the available power of the source.
 - The available power of the source

$$P_{av} = \frac{V^2}{4R_s}$$

- Amplifier is biased two-terminal device, available power:

$$P'_{av} = \frac{V^2}{4(R_s + r_Q)}$$


Two-terminal resistive elements

Available power gain > 1 : negative small-signal resistance

- The available power gain: ratio of P'_{av} and P_{av} :

$$G_P = \frac{P'_{av}}{P_{av}} = \frac{R_s}{R_s + r_Q}$$

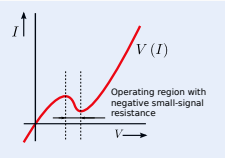- Exceeds unity if the small-signal resistance r_Q of the two-terminal device in the operating point Q has a negative value.
- The tunnel diode is an example of a two-terminal device that has a negative small-signal resistance in a certain operating region.



Nonlinear multi-terminal resistive elements

Multi-terminal, complementary, resistive devices

Complementary multi-terminal resistive devices M_1 and M_2 :

$$M_1 : f_{1\dots n} (V_1 \dots V_n, I_1 \dots I_n) = 0$$

$$M_2 : g_{1\dots n} (V_1 \dots V_n, I_1 \dots I_n) = 0$$

These elements are said to be complementary if:

$$g_{1\dots n} (V_1 \dots V_n, I_1 \dots I_n) = -f_{1\dots n} (-V_1 \dots -V_n, -I_1 \dots -I_n)$$

Nonlinear multi-terminal resistive elements

Two-port representations

Introduction

Nonlinear two-terminal resistors

Nonlinear multi-terminal resistors

Nonlinear resistive two-port representations:

Voltage-controlled representation:	$I_i = I_i(V_i, V_o)$	$I_o = I_o(V_i, V_o)$
Current-controlled representation:	$V_i = V_i(I_i, I_o)$	$V_o = V_o(I_i, I_o)$
Hybrid 1 representation:	$I_i = I_i(V_i, I_o)$	$V_o = V_o(V_i, I_o)$
Hybrid 2 representation:	$V_i = V_i(I_i, V_o)$	$I_o = I_o(I_i, V_o)$
Transfer 1:	$I_o = i_o(V_i, I_i)$	$V_o = V_o(V_i, I_i)$
Transfer 2:	$V_i = V_i(v_o, I_o)$	$I_i = I_i(V_o, I_o)$

Nonlinear multi-terminal resistive elements


Operating point and biasing

- Two-port equations in voltage-controlled notation:

$$I_i = I_i(V_i, V_o)$$

$$I_o = I_o(V_i, V_o)$$

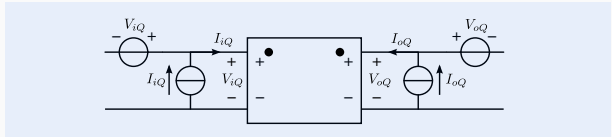- Selection of operating point; relation between bias quantities given by device equations:



- Two-port equations of biased device in voltage-controlled notation:

$$i_i = I_{iQ}(v_i, v_o)$$

$$i_o = I_{oQ}(v_i, v_o)$$

Nonlinear multi-terminal resistive elements

Available power gain of linearized biased nonlinear two-port

Transmission parameter representation:

$$\begin{pmatrix} V_i \\ I_i \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_o \\ I_o \end{pmatrix}$$

$$A = \left. \frac{\partial V_{iQ}(v_o, i_o)}{\partial \tilde{v}_o} \right|_{i_o=0}, \quad B = - \left. \frac{\partial V_{iQ}(v_o, i_o)}{\partial i_o} \right|_{v_o=0}$$

$$C = \left. \frac{\partial I_{iQ}(v_o, i_o)}{\partial v_o} \right|_{i_o=0}, \quad D = - \left. \frac{\partial I_{iQ}(v_o, i_o)}{\partial i_o} \right|_{v_o=0}$$

Available power gain:

$$G_P = \frac{1}{AD + AB/R_s + BC + CDR_s}$$