

# Modeling of Negative Feedback Amplifiers

## Black, Superposition Model, Asymptotic-gain Model

Anton J.M. Montagne

Perscitech B.V.

April 30, 2017

# Introduction

## History of feedback

### Introduction


### Superposition Model

### Asymptotic- gain model

- 1927 Harold Black (1898-1983) built the first negative-feedback amplifier
- Theory concerning stability: Harry Nyquist (1889-1976) and Hendrik Bode (1905-1982)
- 1937 Black's patent for negative feedback awarded.
- Nowadays: widespread use of Black's feedback model
- Not optimally suited for two-step design:
  - ① Design of the ideal transfer: feedback network(s) around nullor(s)
  - ② Design of the *controller(s)* also: *loop amplifier(s)*.

# Introduction

## Black's feedback model

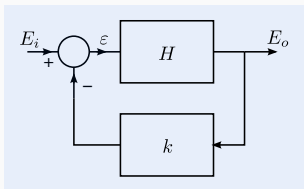

$E_i$  = input quantity

$E_o$  = output quantity

$H$  = gain of high-gain amplifier

$k$  = transfer feedback network

$\varepsilon$  = error signal

$1 + Hk$  = return difference

$Hk$  = return ratio also: *loop gain*

## Input-output transfer

$$\frac{E_o}{E_i} = \frac{1}{k} \left( \frac{Hk}{1 + Hk} \right), \quad \lim_{Hk \rightarrow \infty} \left( \frac{E_o}{E_i} \right) = \frac{1}{k}$$

# Introduction

Black's feedback model

## Not modeled:

- Influence of source and load impedances
- Direct transfer from source to load
- Influence of impedance feedback network

## Suited for design with voltage operational amplifiers:

- High differential and common-mode input impedance
- High common-mode rejection
- Low output impedance

**Model does not facilitate the two-step design approach for  
application-specific negative-feedback amplifiers**

# Selection of the loop gain reference

SLiCAP examples application of Black's feedback model

- Section 6.2.2. in the book, example 6.1 and 6.2
- SLiCAP execute: `~/day5/Exercises5/Exercises5.m`
- Study script and its output: `~/day5/Exercises5/vAmpBlack.m`
- Study script and its output: `~/day5/Exercises5/vAmpBlackF.m`

# Feedback modeling

Hendrik Bode, 1945

- In 1945, Hendrik Bode formulated a feedback theory based on the selection of a controlled source as loop gain reference:  
The *Return Difference*  $F$  and the *Return Ratio*  $T$  for the specific selection of a controlled source can be found from the network matrix equation as:

$$F = 1 + T = \frac{\Delta}{\Delta^0}$$

Where:  $\Delta$  is the determinant of the network matrix and  $\Delta^0$  is the determinant of the network matrix in which the gain of the selected controlled source has been set to 0.

# Feedback modeling

## Stability

- The return ratio or loop gain is a complex transfer function:  $T(s)$ . If its value is larger than unity, we speak of negative, degenerated or corrected feedback.
- Sufficiently stable behavior of the *return difference* requires a certain distance of  $T(s)$  to  $-1$ 
  - *phase margin* and *amplitude margin* tell us about this distance, and thus about the 'amount of stability' with the selected loop gain reference
- However, they do not tell us anything about the actual frequency response of the amplifier:
  - How does the transfer of the amplifier relate to the return difference or to the loop gain for an arbitrarily selected loop gain reference?

# Feedback modeling


Rosenstark

- The asymptotic-gain model, described by Rosenstark provides relations between the return difference and the source to load transfer of an amplifier
  - It is based on the superposition model
  - The expression for the source to load transfer obtained with this model is identical to one obtained from the cofactors of the circuit network
- The asymptotic-gain model facilitates a two-step approach for the design of negative feedback amplifiers in the best possible way:
  - ① Design of the ideal transfer (nullors as controllers)
  - ② Design of the controller



# Superposition Model

## Introduction

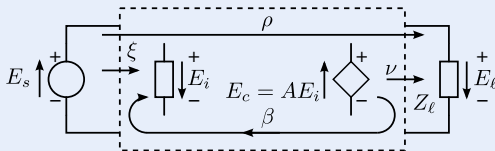

The gain of one arbitrarily selected controlled source of the network is selected as reference variable:


$$A = \frac{E_c}{E_i}$$

$E_c$  = controlled quantity,  $E_i$  = controlling quantity

# Superposition Model
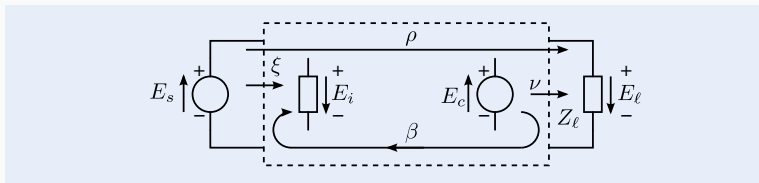
## Basic equations

The controlled source is replaced with an independent source  $E_c$ .



The dependent variables  $E_i$  and  $E_l$  can now be written as a linear combination of the independent variables  $E_s$  and  $E_c$  (superposition).

$$\begin{bmatrix} E_l \\ E_i \end{bmatrix} = \begin{bmatrix} \rho & \nu \\ \xi & \beta \end{bmatrix} \begin{bmatrix} E_s \\ E_c \end{bmatrix}$$

# Superposition Model

Model parameters and source-load transfer

## Model parameters:

- $\rho = \left. \frac{E_\ell}{E_s} \right|_{E_c=0}$  : Direct transfer from source to load
- $\nu = \left. \frac{E_\ell}{E_c} \right|_{E_s=0}$  : Transfer from  $E_c$  to the load
- $\zeta = \left. \frac{E_i}{E_s} \right|_{E_c=0}$  : Transfer from source to driving quantity  $E_i$
- $\beta = \left. \frac{E_i}{E_c} \right|_{E_s=0}$  : Transfer from  $E_c$  to  $E_i$ ; a non-zero value of  $\beta$  indicates the existence of feedback ( $A\beta = \text{loop gain}$ ).

## source-load transfer:

$$A_f = \frac{E_\ell}{E_s} = \rho + \frac{\nu \zeta A}{1 - A\beta}$$

# Asymptotic-gain Model

Model derived from superposition model

Asymptotic-gain is source-load transfer when  $A \rightarrow \infty$ ; with  $\beta \neq 0$  this implies  $A\beta \rightarrow -\infty$ :

$$A_{f\infty} = \lim_{A\beta \rightarrow -\infty} \frac{E_\ell}{E_s} = \rho - \frac{v\zeta}{\beta}$$

Rewrite the source-load transfer in terms of  $A_{f\infty}$ ,  $\rho$  and  $A\beta$ :

$$A_f = A_{f\infty} \frac{-A\beta}{1 - A\beta} + \frac{\rho}{1 - A\beta} = A_{f\infty} \left( \frac{-A\beta}{1 - A\beta} \right) \left( 1 + \frac{\rho}{A_{f\infty}} \frac{1}{1 - A\beta} \right)$$

The contribution of the direct transfer can almost always be neglected: with proper selection of  $A$ ,  $A_{f\infty}$  will equal the ideal gain of the amplifier. This gain will always be larger than the direct transfer!

$$A_f = A_{f\infty} \frac{-A\beta}{1 - A\beta}$$

# Asymptotic-gain Model

Asymptotic-gain versus ideal gain

- Asymptotic gain:  $A_{f\infty} = \rho - \frac{v\xi}{\beta}$
- The ideal gain is the source load transfer when the controller has nullor properties
- Consider the controlling quantity of the loop gain reference is taken at the input port of the controller:


$$E_i = \frac{\xi}{1 - A\beta} E_s, \quad \lim_{A\beta \rightarrow \infty} E_i = 0$$

- If  $A\beta \rightarrow \infty$  results in both zero voltage across the input port and zero current through the input port of the controller, the asymptotic gain equals the ideal gain (controller has nullor properties)
- We then have a two-step design approach for the negative feedback amplifier!
- This requires proper selection of  $A$ !


# Example voltage amplifier

Negative feedback amplifier with current feedback operational amplifier

## Amplifier + Opamp model:

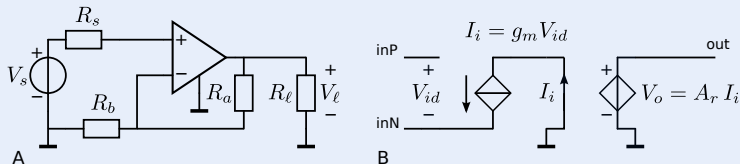

## Complete small-signal model:

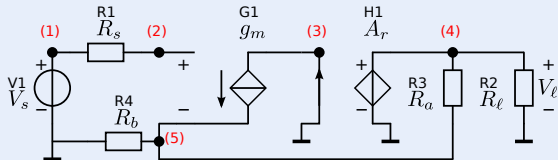

# Selection of the loop gain reference

## SLiCAP example with current-feedback operational amplifier

- Section 6.3.3 in the book, example 6.3
- SLiCAP execute: `~/day5/Exercises5/Exercises5.m`
- Study script and its output: `~/day5/Exercises5/cfbVamp.m`

# Asymptotic-gain Model

## Conclusions

- ① The asymptotic-gain model gives exactly the same results for the source-load transfer as MNA, this result does not depend on the choice of the reference variable
- ② If the reference variable is selected in such a way that the active part of the amplifier obtains nullor properties for  $A\beta \rightarrow \infty$ :
  - ① The asymptotic-gain equals the ideal gain
  - ② If the reference variable has been selected properly, the error of the transfer with respect to this ideal gain can be described solely by the return ratio.
- ③ In that case the design of a negative feedback amplifier can be performed in two successive and independent steps:
  - ① Design of the ideal gain (feedback topology)
  - ② Design of the loop gain function  $A\beta$  such that the error with respect to the ideal gain is sufficiently small. All errors with respect to the ideal gain can then be obtained from  $A\beta$ !



# Asymptotic-gain Model

The servo function

- The servo function  $F_s(s)$  is a measure for the correspondence between the gain and the asymptotic gain.
- It is defined as the ratio between the source to load transfer  $A_f$  and the asymptotic gain  $A_{f\infty}$ .

$$F_s = \frac{A_f}{A_{f\infty}} = \frac{-A\beta}{1 - A\beta}$$

- Its ideal value is 1.
- The relative error of the gain with respect to the asymptotic gain is the deviation of this servo function from unity:

$$\delta = F_s - 1 = \frac{-1}{1 - A\beta} \approx \frac{1}{A\beta}$$

- Please notice: negative feedback:  $A\beta < 0$ . Hence  $A\beta = -T$ , where  $T$  is the return ratio according to the definition given by Bode.

# Asymptotic-gain Model

## Mismatch between ideal gain and the asymptotic-gain

- If the reference variable has been selected properly there can still be a mismatch between the ideal gain and the asymptotic-gain
- Parasitic impedances between the input port and/or the output port of the nullor and ground may compromise the two-port port conditions.
- Section 6.3.3 in the book, example 6.4
- SLiCAP execute: `~/day5/Exercises5/Exercises5.m`
- Study script and its output: `~/day5/Exercises5/cfbVampExtended.m`

# Asymptotic-gain Model

## Impedance model

- The asymptotic-gain model can also be used for the design of accurate, finite, non-zero port impedances
- Realization of such impedances requires both series and shunt feedback at an amplifier port
- If a port is shorted, the shunt feedback is inactive and the loop gain equals  $A\beta_{sc}$
- If a port is left open, the series feedback is inactive and the loop gain equals  $A\beta_o$
- The port impedance can be written in terms of its asymptotic-gain  $Z_{f\infty}$  and the two loop gains  $A\beta_{sc}$  and  $A\beta_o$ .

# Asymptotic-gain Model

## Impedance model

- Loop gain with port terminals shorted:  $A\beta_{sc}$
- Loop gain with port terminals left open:  $A\beta_o$
- Port impedance of amplifier concept with nullor:  $Z_{f\infty}$
- Actual port impedance:

$$Z_f = Z_{f\infty} \frac{A\beta_o}{1 - A\beta_o} \frac{1 - A\beta_{sc}}{A\beta_{sc}}$$

- We have two servo functions, one applies to the open port and the other to the shorted port.

# Asymptotic-gain model

Influence of negative feedback on the port impedances of single-loop  
feedback amplifiers

- $Z_{f\infty}$  = ideal value of the port impedance; single loop negative feedback:
  - parallel feedback at the port  $Z_{f\infty} = 0$
  - series feedback at the port  $Z_{f\infty} = \infty$
- Usually no need for studying the port impedance  $Z_f$  of single-loop negative feedback amplifiers:
  - All error contributions including those due to non ideal port impedances are included in  $A\beta$ .
- If desired, the port impedance with feedback  $Z_f$  can be found from impedance model:
  - Shunt feedback at the port:  $A\beta_{sc} = 0$ :  $Z_f = \frac{\rho}{1-A\beta_o}$
  - Series feedback at the port:  $A\beta_o = 0$ :  $Z_f = \frac{\rho}{1-A\beta_{sc}}$
  - $\rho$  is the port impedance with the loop gain reference set to zero.

# Impedance model

Obtain output impedance operational amplifier from its 'closed-loop' value and the loop gain

- Shunt feedback at the port:

$$Z_f = \frac{\rho}{1 - A\beta_o}$$

$\rho$  is the port impedance  $Z_x$  with the loop gain reference set to zero, we obtain:

$$\begin{aligned} Z_x &= Z_f (1 - A\beta_o) \\ |A\beta_o| &\gg 1 \\ &\approx -A\beta_o Z_f \end{aligned}$$