

CMOS Controller Design

The method

From single device to multiple-stage controller

Understand basic amplification with single transistor

- The biased CS stage
- Behavior of the intrinsic CS stage (ideal drive and load conditions)
 - * Static nonlinear behavior and design of voltage and current drive capability
 - * Dynamic nonlinear behavior
 - * Dynamic small-signal behavior
 - * Noise behavior
- Behavior of the CS stage when connected between a source and a load
 - * Small-signal dynamic behavior
 - * Noise behavior and optimization of the noise behavior

Understand in which way the performance of a stage can be changed through application of error reduction techniques

- Application of balancing techniques: differential pair and push-pull stage
- Application of direct negative feedback: the CD and the CG stage
- Application of indirect negative feedback: the current mirror and the voltage mirror

Putting it all together

- The cascode stage and the balanced cascode stage
- Controller design strategy

CS basic amplifier stage


The biased CS stage

Output port biased for performance

- Input stage: noise
- Output stage: drive capability
- Intermediate stages:
 - * Drive capability
 - * Contribution to:
 - LP product
 - Differential error to gain ratio

Bias sources at input port depend on device characteristics

 - Can be determined by SPICE
- Biasing of particular device at simulation temperature correct for all resistive port terminations






Behavior of the intrinsic CS stage

Static nonlinear behavior

- All curves pass through the origin
- Current sink capability exceeds current source capability (latter one limited by bias current)

   - Modeling of nonlinear effects is shown
- Other static transfers are not shown:
 - * Input resistance is infinite
 - * DC current gain is infinite
 - * DC current to voltage transfer is infinite



Optimization of the noise performance of a CS stage for a resistive source and for high frequencies (no 1/f noise)

$$S_{v_{nR_s}} = 4kTR_s$$


$$S_{i_n} = 4kTn\Gamma g_m \left(1 + \frac{f_c}{f}\right)$$

$$S_{i_{nG}} = 2qIG$$


$$B = -\frac{1}{g_m}$$

$$D = -\frac{sC_{gs}}{g_m} = -\frac{s}{2\pi f_T}$$


Dynamic nonlinear behavior

 

Noise behavior

 

 - Transformation into equivalent input sources:



Device scaling

MOS Scaling parameters



- W width
- L length
- n fingers
- m devices

- Effective width: $W_{eff} = 2nmW$ source terminal always shared

- * Current-drive capability @ available V_{gs}
- * Optimization of noise performance
- * Optimization of device matching

Behavior of the CS stage between source and load

  Small-signal dynamic behavior when driven/terminated from/with parallel RC




Qualitative description of the dynamic behavior (transimpedance gain)

 1. If $C_g = 0$, the circuit has two poles; associated with the two RC networks.
2. If C_g is small with respect to the other capacitances, C_g will not affect the product of the poles
 - The sum of the poles will be increased (Miller effect): one pole is closer to the origin, thus the other moves towards a higher frequency. This is called pole-splitting (due to capacitive feedback)

- A positive zero is found at: $s = \frac{g_m}{C_{gd}}$

Pole-splitting can be used for frequency compensation. Undesired pole-splitting may be a cause for bandwidth reduction in a feedback amplifier. This is the case if the high frequency pole is split out of the dominant group.



$$S_{V_n} = 4kT \left(R_s + \frac{n\Gamma}{g_m} \right) \left(1 + \frac{f_c^2}{f^2} \right)$$



$$F_{opt} = \left(1 + \frac{n\Gamma}{\sqrt{3}f_T} \sqrt{\frac{f_{max}^3 - f_{min}^3}{f_{max} - f_{min}}} \right)^2$$

- Inversion coefficient close critical inversion
- find optimum width and best possible noise figure

- For frequencies at which the 1/f noise cannot be ignored, find optimum current and geometry through simulation.
- Lower 1/f corner frequency
 - * Increase both W and L
 - * Cut-off frequency will drop with square of L

Balanced stages

Anti-series stage: differential pair

  

Complementary parallel stage: push-pull stage

Topology

- Can be used as 4-terminal with split-signal output, but not a natural two-port

Biasing


- Common-mode voltage sources only
- Even terms cancel
- Expanding current characteristic
- Imperfect balancing PMOS and NMOS

Small-signal dynamic

- Transmission coefficients A and D equal those of constituting elements
- Coefficient B half
- Coefficient C twice as large



Noise Behavior

 - Voltage noise spectrum half that of constituting transistors
- Current noise spectrum twice as large



Local feedback stages

Basic nullor implementations

  

The CD stage or source follower

Non-energetic feedback unity-gain voltage amplifier

- Behavioral modifications through application of negative feedback:
 - * Nonenergetic: equivalent input noise sources equal those of its CS stage controller
 - * Parallel voltage sensing: decreases output impedance
 - * Series voltage comparison: increases input impedance
- Feedback not effective if sensing or comparison not possible:
 - * Output shorted
 - * Input current-driven
- Back-gate effect reduces loop gain
- Poles may be complex with capacitive load

Behavioral modifications

Topology

- 4-terminal
- Behavior approximates that of natural two-port

Biasing


- Common-mode current sources only

Large signal static behavior

- Even terms cancel
- Limiting current characteristic



Small-signal dynamic

 - Transmission coefficients A and D equal those of constituting elements
- Coefficient B twice as large
- Coefficient C half



Noise Behavior

  - Voltage noise spectrum twice as large
- Current noise spectrum half that of individual transistors



Putting it all together

Input stage

CS, CE, balanced version, preferably cascode

- Best possible nullor approximation
- Best possible contribution to LP product and DG ratio
- Determine device geometry range and operating current range that satisfies noise requirements
- * Model the controller as a nullor with the noise sources of the input device, with geometry and operating current as design parameters


Intermediate stages

CS, CE, balanced version, preferably cascode

- Best possible nullor approximation
- Best possible contribution to LP product and DG ratio

Interconnection of stages

 Maintain two-port conditions for the controller



Biasing

Method: maintain DC coupling between stages

- Redirect bias current sources via the power supply
- Minimize the number of floating voltage sources (level shifts)
- Apply error reduction techniques for improvement of
 - * Common-mode biasing
 - Common-mode feedback
 - * Biasing of stages
 - Model-based feedback (indirect feedback)
 - * Reduction of over-all operating point drift and in accuracy
 - AC coupling
 - AC coupling + over-all biasing feedback

General: maintain two-port conditions for the controller

- Avoid signal current flowing to the power supply or ground
- Ensure a low impedance for supply voltages and minimize supply noise, particularly in cases in which both the ground and the supply node are used as signal reference

Output stage

CS, CE, balanced version, preferably cascode

- Best possible nullor approximation
- Best possible contribution to LP product and DG ratio
- Use complementary-parallel stage for improved power efficiency
- Determine device geometry range and operating current range that satisfies the drive requirements
- Also determine the drive conditions for this stage

Number of stages

Single stage controller

- If device geometry and operating requirements for input and output stage overlap

Two-stage controller

- If the drive requirements for the output stage overlap with the operating conditions for the input stage
- If the LP product of the loop gain of this two-stage solution satisfies the bandwidth requirements
- If the differential error to gain ratio of this two-stage solution satisfies the distortion requirements

Multiple-stage controller

- If conditions for a two-stage controller are not satisfied
- Consider application of passive local feedback stages:
 - * Increase loop gain without adding a dominant pole