

Structured Electronic Design

Determination of OpAmp GB-product requirement

Procedure for finding required GB product OpAmp

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically

a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed
3. Derive an expression for the loop gain (mixed symbolic, numeric)

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed
3. Derive an expression for the loop gain (mixed symbolic, numeric)
4. Determine the loop gain-poles product (and its order) from this expression

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed
3. Derive an expression for the loop gain (mixed symbolic, numeric)
4. Determine the loop gain-poles product (and its order) from this expression
5. Solve GB from: $LP_n - (2\pi B_f)^n = 0$ $B_f = \text{required bandwidth in [Hz]}$

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed
3. Derive an expression for the loop gain (mixed symbolic, numeric)
4. Determine the loop gain-poles product (and its order) from this expression
5. Solve GB from: $LP_n - (2\pi B_f)^n = 0$ B_f = required bandwidth in [Hz]
6. Find show stopper value with input capacitances and output resistance set to zero

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed
3. Derive an expression for the loop gain (mixed symbolic, numeric)
4. Determine the loop gain-poles product (and its order) from this expression
5. Solve GB from: $LP_n - (2\pi B_f)^n = 0$ B_f = required bandwidth in [Hz]
6. Find show stopper value with input capacitances and output resistance set to zero
7. Example 11.2 (study this example during next instruction)

Procedure for finding required GB product OpAmp

1. Make a model of the OpAmp
model relevant parameters for dynamic behavior symbolically
 - a. DC gain and single pole: $A_v = \frac{A_0}{1 + s \frac{A_0}{2\pi GB}}$
 - b. Differential-mode and common-mode input capacitances
 - c. Output resistance
2. Model the amplifier: use numeric values for parameters that have been designed
3. Derive an expression for the loop gain (mixed symbolic, numeric)
4. Determine the loop gain-poles product (and its order) from this expression
5. Solve GB from: $LP_n - (2\pi B_f)^n = 0$ B_f = required bandwidth in [Hz]
6. Find show stopper value with input capacitances and output resistance set to zero
7. Example 11.2 (study this example during next instruction)

SLiCAP functions for determination of the bandwidth

```
gainType('loopgain');      % defines the gain type
dataType('laplace');        % defines the data type
simType('numeric');         % substitutes parameters before execution
lgRef('E1');                % defines the loop gain reference

loopgain = execute();
loopGainRational = loopgain.results(1);
transferCoeffs = coeffsTransfer(loopGainRational);
numCoeffs = transferCoeffs(1);
denomCoeffs = transferCoeffs(2);
servoData = findServoBandwidth(loopGainRational);

help < functionName >    % displays help on a function
```