
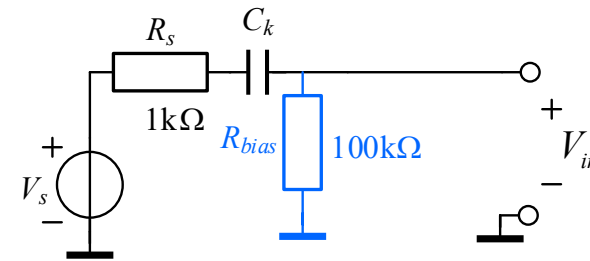


# Exercise 1\_8

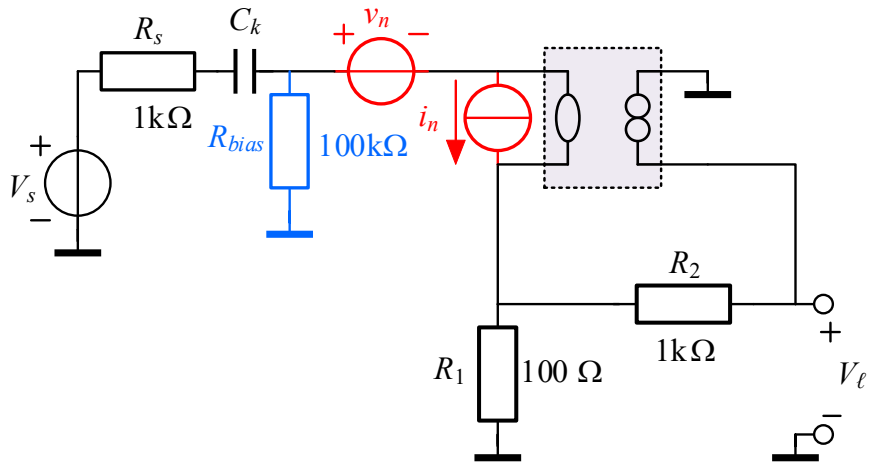

$$H(s) = \frac{s(\dots)}{(\dots)} = \frac{s(\dots)}{1 + (R_s + R_{bias})sC_k} = \frac{(R_{bias})sC_k}{1 + (R_s + R_{bias})sC_k}$$


Propose a reasonable value for  $C_k$  considering the bandwidth requirements.

Is there a zero?  $s = 0$

Is there a pole? 1 pole at:  $s = \frac{1}{(R_s + R_{bias})C_k}$  ← Should be below 50Hz.  $R_{bias}$  much larger than  $R_s$ .

What is the transfer for  $s \rightarrow \infty$ ?  $H(\infty) = \frac{R_{bias}}{R_s + R_{bias}}$
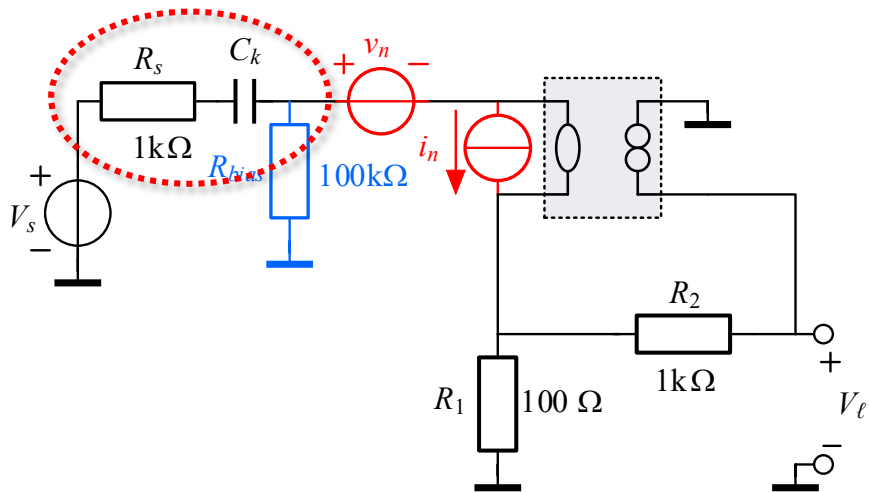
$$C_{k,BW} = \frac{1}{R_{bias} 2\pi f_{\min}} = \frac{1}{10^5 \cdot 2\pi 50} \approx 3.2 \cdot 10^{-8}$$



$$R_s = \left| \frac{1}{sC_{k,noise}} \right|$$

$$C_{k,noise} = \frac{1}{2\pi f_{min} R_s} = \frac{1}{2\pi 50 \cdot 10^3} \approx 3.2 \cdot 10^{-6}$$

$C_k$  converts noise current  $i_n$  into an equivalent voltage source.

$R_s$  converts noise current  $i_n$  into an equivalent voltage source. (we neglect the influence of  $R_1$  and  $R_2$ )

Proposal:  $C_k$  and  $R_s$  have equal impedance at 50Hz for equal contribution.

1 pole at:  $s = \frac{1}{(R_s + R_{bias})C_k}$

Should be below 50Hz.

Conclusion: Noise requirements can put a harsher constrain on the value of  $C_k$  than the bandwidth requirements.

*Of course definite conclusions can only be drawn when the magnitude of all noise sources is known, because then the impact of  $C_k$  on the magnitude of the total equivalent noise source power at the input can be evaluated.*

$$C_{k,BW} = \frac{1}{R_{bias} 2\pi f_{min}} = \frac{1}{10^5 \cdot 2\pi 50} \approx 3.2 \cdot 10^{-8}$$