

EE4109: Agenda (lecture 13)

1. The active antenna design

Recap

SLiCAP/LTSpice design of two-stage amplifier

Frequency compensation two-stage amplifier

"Back of the envelope" estimation

"What ifs?"

2. The specs revisited

3. Homework

